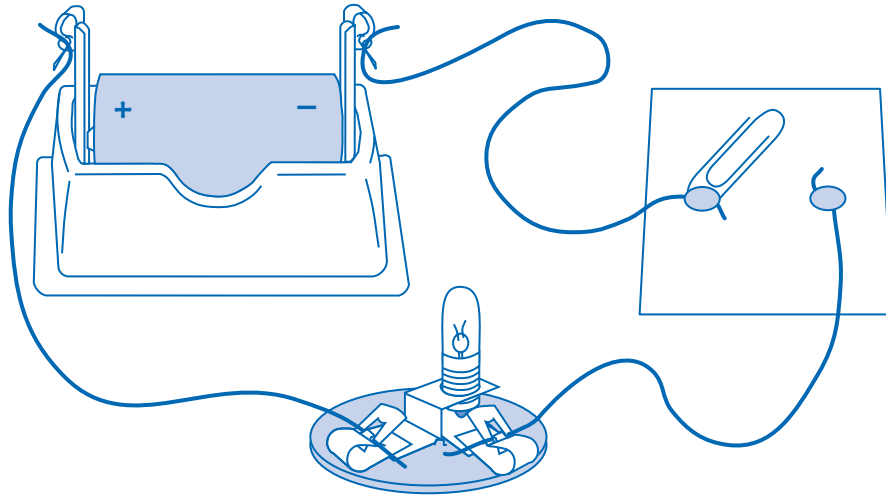


A Paper Clip Switch

Make this circuit.



1. What happens when the paper clip touches the other fastener?

2. What happens when you move the paper clip away from the fastener?
