
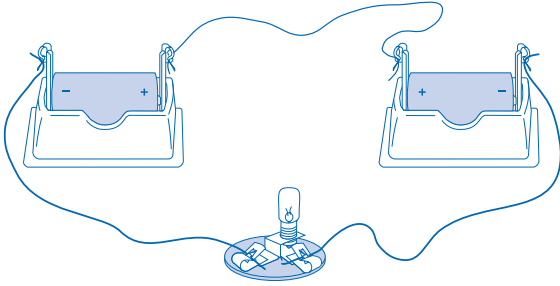


Circuit Experiments

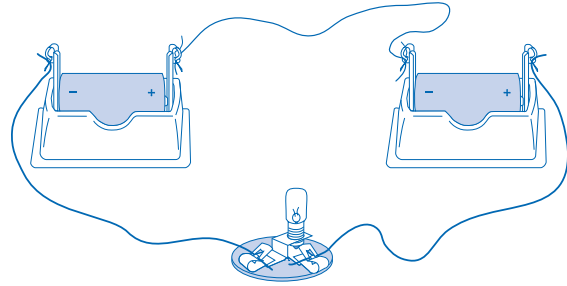1. Circle the circuit that will light the bulb.




Circuit A




Circuit B

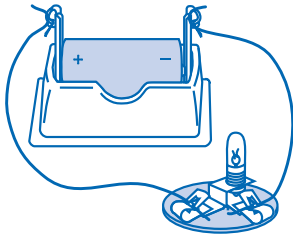2. Circle the circuit that will light the bulb.



Circuit C

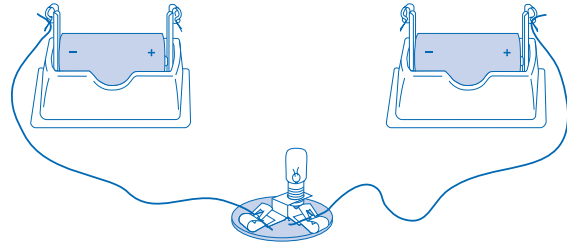

Circuit D

3. Which of the two bulbs will shine brighter? Color that bulb yellow.